

# LATTICE WATERING

## Handout

Christian Müller, Jonas Heinemann, Kaan Dönmez, Valentin Pickel

Software Project on Internet Communication  
Summer Term 2022  
Freie Universität Berlin

May 16, 2022 (latest version)

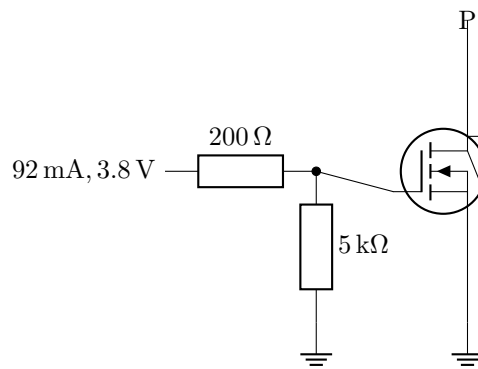


Figure 1: Circuit for the pump P.

Thus, we obtain:

$$I_2 = \frac{5 \text{ V}}{200 \Omega} = 25 \text{ mA}$$

And:

$$I_3 = \frac{5 \text{ V}}{200 \Omega} = 25 \text{ mA}$$